

Microelectronics Circuit Analysis and Design

Homework(15th)

Yuejin Xie U202210333

Nov 15th, 2023

15.15 Consider the bandpass filter in Figure P15.15.(a) Show that the voltage transfer function is

$$A_v(s) = \frac{v_O}{v_I} = \frac{-1/R_4}{(1/R_1) + sC + 1/(sCR_2R_3)}$$

(b) For $C = 0.1\mu\text{F}$, $R_1 = 85\text{ k}\Omega$, $R_2 = R_3 = 300\Omega$, $R_4 = 3\text{ k}\Omega$, and $R_5 = 30\text{ k}\Omega$, determine:
 (i) $|A_v(\text{max})|$; (ii) the frequency f_o at which $|A_v(\text{max})|$ occurs; and (iii) the two 3 dB frequencies.

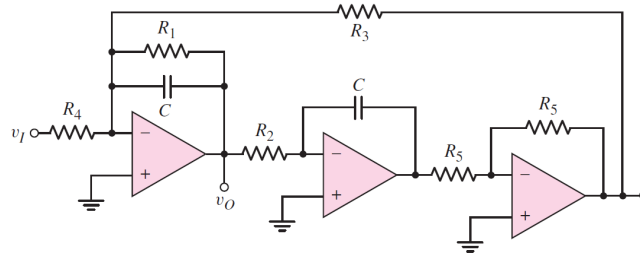


Figure 1: Problem 15.15

Solution:

(a) Because of "KCL", and virtual open and short, we have equation as follow:

$$\begin{cases} \frac{v_I}{R_4} = -\frac{v_2}{R_3} - \frac{v_o}{R_1 \parallel (\frac{1}{sC})} \\ \frac{v_o}{R_2} = -\frac{v_1}{(\frac{1}{sC})} \\ \frac{v_1}{R_5} = -\frac{v_2}{R_5} \end{cases} \Rightarrow A_v(s) = \frac{v_O}{v_I} = \frac{-1/R_4}{(1/R_1) + sC + 1/(sCR_2R_3)}$$

(b) $C = 0.1 \mu\text{F}$, $R_1 = 85 \text{ k}\Omega$, $R_2 = R_3 = 300 \Omega$, $R_4 = 3 \text{ k}\Omega$, and $R_5 = 30 \text{ k}\Omega$, Now

$$\begin{aligned} A_v(s) = \frac{v_o}{v_i} &= \frac{-1/R_4}{(1/R_1) + sC + 1/(sCR_2R_3)} = -\frac{R_1}{R_4} \cdot \frac{1}{1 + sR_1C + \frac{R_1}{sCR_2R_3}} \\ &= -\frac{R_1}{R_4} \cdot \frac{1}{1 + j(\omega R_1C - \frac{R_1}{\omega CR_2R_3})} \\ \Rightarrow |A_v(j\omega)| &= \frac{R_1}{R_4} \cdot \frac{1}{\sqrt{1 + (\omega R_1C - \frac{R_1}{\omega CR_2R_3})^2}} \end{aligned}$$

(i) When $\omega R_1C - \frac{R_1}{\omega CR_2R_3} = 0$, $|A_v(j\omega)|_{\max} = 28.33$

(ii) $\omega = \frac{1}{C\sqrt{R_1R_2}}$, $f_o = \frac{\omega}{2\pi} = 5.31 \text{ kHz}$

(iii) For 3dB frequencies, we have equation:

$$(\omega R_1C - \frac{R_1}{\omega CR_2R_3})^2 = 1, f = \frac{\omega}{2\pi} \Rightarrow f = 5.32 \text{ kHz}, 5.30 \text{ kHz}$$

15.17 For each of the circuits in Figures P15.17, derive the expressions for the voltage transfer function $T(s) = V_o(s)/V_i(s)$ and the cutoff frequency $f_{3\text{dB}}$.

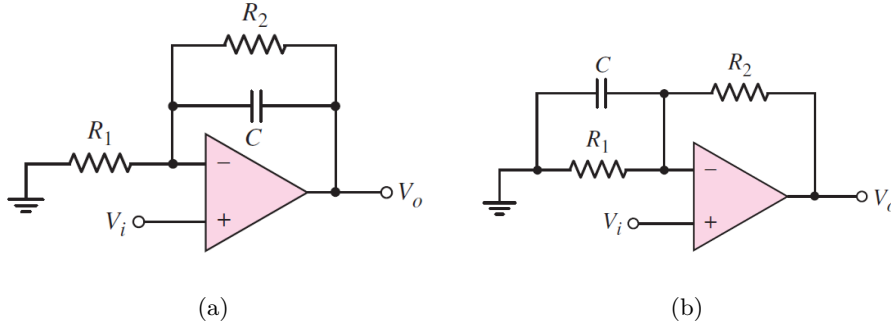


Figure 2: Problem 15.17

Solution:

(a) Because of "KVL", and virtual open and short, we have equation:

$$\begin{aligned} T(s) = V_o(s)/V_i(s) &= \frac{R_1 + R_2 \parallel \frac{1}{sC}}{R_1} = \left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1 + s(R_1 \parallel R_2)C}{1 + sR_2C} \\ \Rightarrow f_H &= \frac{1}{2\pi R_2C}, f_L = \frac{1}{2\pi(R_1 \parallel R_2)C} \end{aligned}$$

(b) Because of "KVL", and virtual open and short, we have equation:

$$\Rightarrow T(s) = V_o(s)/V_i(s) = \frac{R_2 + R_1 \parallel \frac{1}{sC}}{R_1 \parallel \frac{1}{sC}} = \frac{R_2 + R_1}{R_1} \cdot (1 + s(R_1 \parallel R_2)C)$$

$$\Rightarrow f = \frac{1}{2\pi(R_1 \parallel R_2)C}$$

15.46 Consider the Schmitt trigger in Figure P15.46. Assume the saturated output voltages are $\pm V_P$. (a) Derive the expression for the crossover voltages V_{TH} and V_{TL} . (b) Let $R_A = 10 \text{ k}\Omega$, $R_B = 20 \text{ k}\Omega$, $R_1 = 5 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $V_P = 10 \text{ V}$, and $V_{REF} = 2 \text{ V}$. (i) Find V_{TH} and V_{TL} . (ii) Sketch the voltage transfer characteristics.

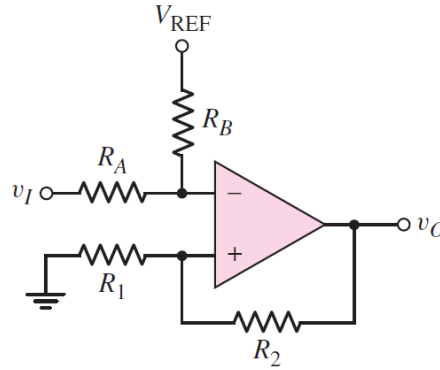


Figure 3: Problem 15.46

Solution:

(a) For $V_O = +V_P$:

$$\frac{R_A}{R_A + R_B} V_{REF} + \frac{R_B}{R_A + R_B} V_{TH} = \frac{R_1}{R_1 + R_2} V_P \Rightarrow V_{TH} = \left(\frac{R_A + R_B}{R_1 + R_2} \right) \left(\frac{R_1}{R_B} \right) V_P - \left(\frac{R_A}{R_B} \right) V_{REF}$$

For $V_O = -V_P$:

$$V_{TL} = - \left(\frac{R_A + R_B}{R_1 + R_2} \right) \left(\frac{R_1}{R_B} \right) V_P - \left(\frac{R_A}{R_B} \right) V_{REF}$$

(b) $R_A = 10 \text{ k}\Omega$, $R_B = 20 \text{ k}\Omega$, $R_1 = 5 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $V_P = 10 \text{ V}$, and $V_{REF} = 2 \text{ V}$, so

(i)

$$V_{TL} = -4\text{V}, V_{TH} = 2\text{V}$$

(ii)

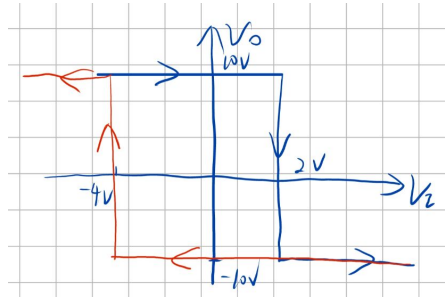


Figure 4: Problem 15.46 voltage transfer characteristics

15.47 The saturated output voltages are $\pm V_P$ for the Schmitt trigger in Figure P15.47. (a) Derive the expressions for the crossover voltages V_{TH} and V_{TL} (b) If $V_P = 12V$, $V_{REF} = -10V$, and $R_3 = 10k\Omega$, find R_1 and R_2 such that the switching point is $V_S = -5V$ and the hysteresis width is $0.2V$. (c) Sketch the voltage transfer characteristics.

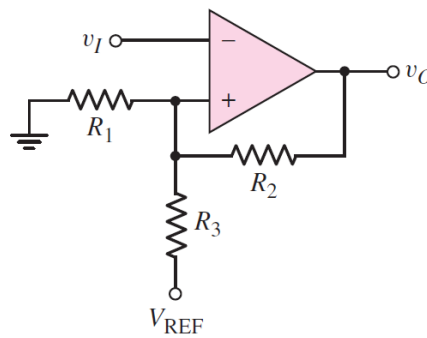


Figure 5: Problem 15.47

Solution:

(a) For $V_O = V_P$:

$$\frac{V_O - V_{TH}}{R_2} + \frac{V_{REF} - V_{TH}}{R_3} = \frac{V_{TH}}{R_1} \Rightarrow V_{TH} = \frac{\frac{V_{REF}}{R_3} + \frac{V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

For $V_O = -V_P$:

$$\frac{V_O - V_{TH}}{R_2} + \frac{V_{REF} - V_{TH}}{R_3} = \frac{V_{TH}}{R_1} \Rightarrow V_{TH} = \frac{\frac{V_{REF}}{R_3} - \frac{V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}$$

(b) Equations as follow:

$$\begin{cases} \frac{\frac{V_{REF}}{R_3}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)} = -5 \\ \Delta V_T = V_{TH} - V_{TL} = \frac{\frac{2V_P}{R_2}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)} = 0.2 \end{cases} \Rightarrow R_1 = 10.17\text{k}\Omega, R_2 = 600\text{k}\Omega$$

(c) $V_{TL} = -5.1\text{V}, V_{TH} = -4.9\text{V}$

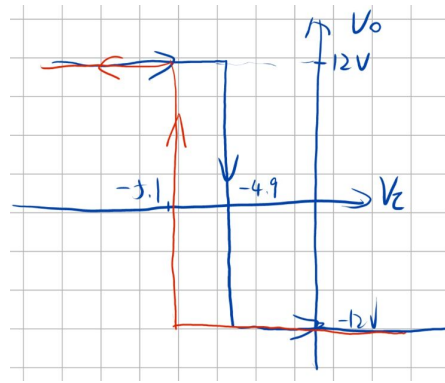


Figure 6: Problem 15.47 voltage transfer characteristics

15.48 (a) Plot the voltage transfer characteristics of the comparator circuit in Figure P15.48 assuming the open-loop gain is infinite. Let the reverse Zener voltage be $V_Z = 5.6$ V and the forward diode voltage be $V_\gamma = 0.6$ V. (b) Repeat part (a) for an open-loop gain of 10^3 . (c) Repeat part (a) for 2.5 V applied to the inverting terminal of the comparator.

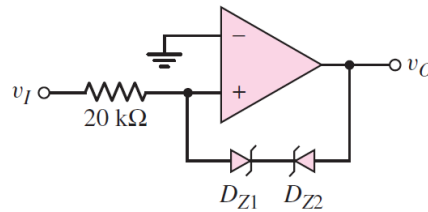


Figure 7: Problem 15.48

Solution:

(a) case 1: $|V_P| < 6.2\text{V}$, the Diodes are open:

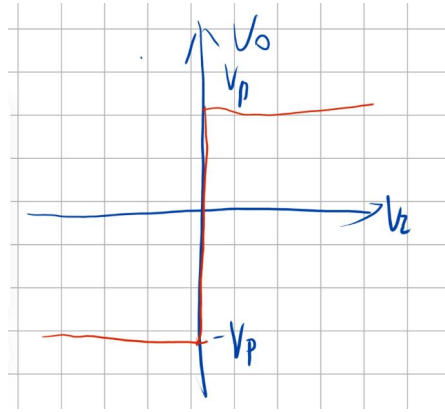


Figure 8: Problem 15.48

case 2: $|V_P| > 6.2\text{V}$, the one of the Zener Diodes work, $|V_O| = 6.2\text{V}$ and input can be ignored

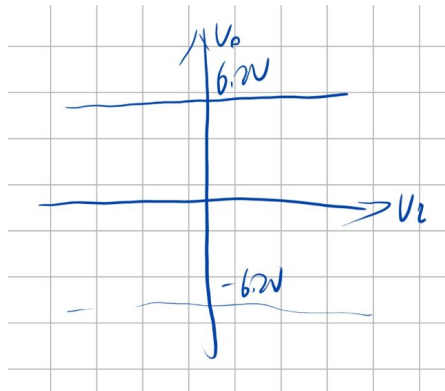


Figure 9: Problem 15.48

(b) Same as (a)

(c) when $V_O < 8.7\text{ V}$ and $V_O > 3.7\text{ V}$, work as comparator. Otherwise the input has no control

15.79 The voltage regulator shown in Figure P15.79 is a variable voltage, 0 to 5 A power supply. The transistor parameters are $\beta = 80$ and $V_{BE(\text{on})} = 0.7\text{ V}$. The op-amp has a finite open-loop gain of $A_{OL} = 5 \times 10^3$. The zero-current Zener voltage is $V_{ZO} = 5.6\text{ V}$ and the Zener resistance is $r_z = 12\Omega$. (a) For $I_Z = 12\text{mA}$, find R_1 . (b) Determine the range of output voltage as the potentiometer R_3 is varied. (c) If the potentiometer is set such $x = 1$, determine R_o of the op-amp is zero.

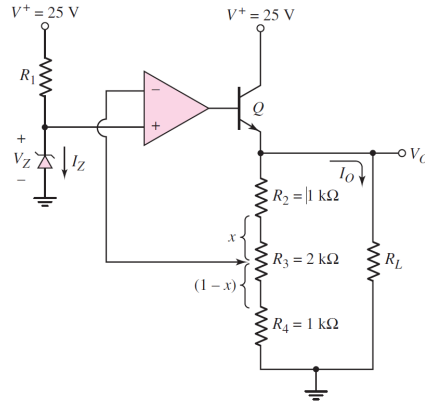


Figure 10: Problem 15.79

Solution:

(a)

$$R_1 + r_z = \frac{V^+}{I_Z} = \frac{25}{12} = 2.0833\text{k}\Omega \Rightarrow R_1 = 2.0713\text{k}\Omega$$

(b) $V^+ = V_Z + I_Z = 5.744\text{V}$

If $x = 0$,

$$V^+ = \left(\frac{R_3 + R_4}{R_2 + R_3 + R_4} \right) V_O \Rightarrow V_O = 7.659\text{V}$$

If $x = 1$,

$$V^+ = \left(\frac{R_4}{R_2 + R_3 + R_4} \right) \cdot V_O \Rightarrow V_O = 22.976\text{V}$$

So $7.659 \leq V_O \leq 22.976\text{V}$

(c)???

15.80 The parameters of the transistor in Figure P15.80 are $\beta = 80$ and $V_{EB(on)} = 0.6$ V. The Zener diode is ideal with $V_Z = 6.8$ V and the op-amp is ideal. (a) Determine the range of load resistance R_L such that the load current is a constant. What is the value of the constant load current? (b) If the Zener diode has a resistance $r_z = 20\Omega$ and the power supply is in the range $16 \leq V_S \leq 20$ V, determine the range in output current for $R_L = 5\text{k}\Omega$.

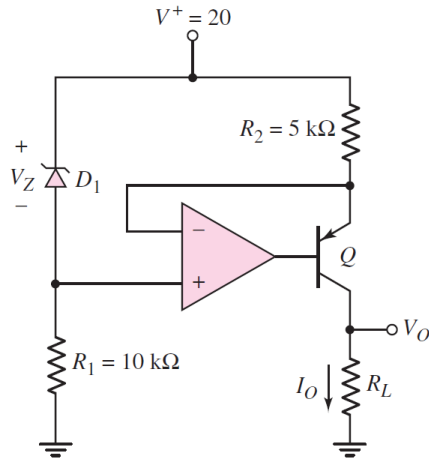


Figure 11: Problem 15.80

Solution:

(a)

$$I_O = \left(\frac{\beta}{1 + \beta} \right) \cdot \frac{V_Z}{R_2} = 1.343 \text{mA}$$

$$R_L(\text{max}) = \frac{V^+ - V_Z - V_{BE}(\text{on})}{I_O} = 9.38 \text{k}\Omega$$

(b) For $V_S = 16 \text{V}$

$$I_O = \left(\frac{\beta}{1 + \beta} \right) \frac{V_S - \frac{R_1}{R_1 + r_Z}(V_S - V_Z)}{R_2} = 1.3484 \text{mA}$$

For $V_S = 16 \text{V}$

$$I_O = \left(\frac{\beta}{1 + \beta} \right) \frac{V_S - \frac{R_1}{R_1 + r_Z}(V_S - V_Z)}{R_2} = 1.3468 \text{mA}$$