

Microelectronics Circuit Analysis and Design

Homework(10th)

Yuejin Xie U202210333

Oct 23rd, 2023

8.24 Consider the class-B output stage with complementary MOSFETs shown in Figure P8.24. The transistor parameters are $V_{TN} = V_{TP} = 0$ and $K_n = K_p = 0.4\text{mA}/N^2$. Let $R_L = 5\text{ k}\Omega$. (a) Find the maximum output voltage such that M_n remains biased in the saturation region. What are the corresponding values of i_L and v_I for this condition? (b) Determine the conversion efficiency for a symmetrical sine-wave output signal with the peak value found in part (a).

 


Figure 1: Problem 8.24

8.29 An enhancement-mode MOSFET class-AB output stage is shown in Figure P8.29. The threshold voltage of each transistor is $V_{TN} = -V_{TP} = 1\text{ V}$ and the conduction parameters of the output transistors are $K_{n1} = K_{p2} = 5\text{ mA}/V^2$. Let $I_{\text{Bias}} = 200\text{ }\mu\text{ A}$. (a) Determine $K_{n3} = K_{p4}$ such

that the quiescent drain currents in M_1 and M_2 are 5 mA. (b) Using the results of part (a), find the small-signal voltage gain $A_v = dv_O/dv_I$ evaluated at: (i) $v_O = 0$, and (ii) $v_O = 5\text{V}$.

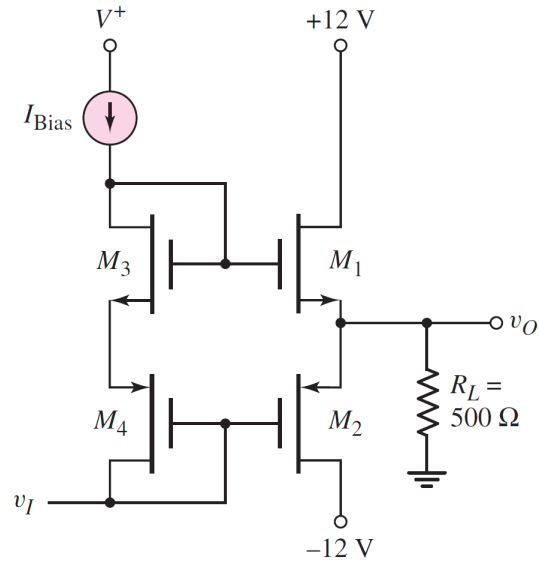


Figure 2: Problem 8.29