

Microelectronics Circuit Analysis and Design

Homework(11st)

Yuejin Xie U202210333

Oct 23rd, 2023

10.44 Consider the MOSFET current-source circuit in Figure P10.44 with $V^+ = +2.5\text{V}$ and $R = 15\text{ k}\Omega$. The transistor parameters are $V_{TN} = 0.5\text{V}$, $k'_n = 80\mu\text{A/V}^2$, $W/L = 80\mu\text{A/V}^2$, $W/L = 6$, and $\lambda = 0$. Determine I_{REF} , I_O , and $V_{DS2}(\text{sat})$.

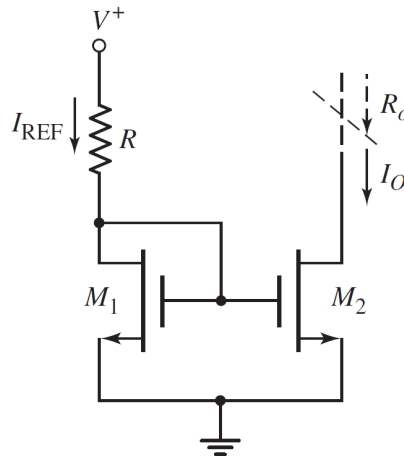


Figure 1: Problem 10.44

10.54 The transistor circuit shown in Figure P10.54 is biased at $V^+ = +5\text{V}$ and $V^- = -5\text{ V}$. The transistor parameters are $V_{TP} = -1.2\text{V}$, $k'_p = 80\mu\text{A/V}^2$, $\lambda = 0$, $(W/L)_1 = (W/L)_2 = 25$, and $(W/L)_3 = (W/L)_4 = 4$. Determine I_{REF} , I_O , and $V_{SD2}(\text{sat})$.

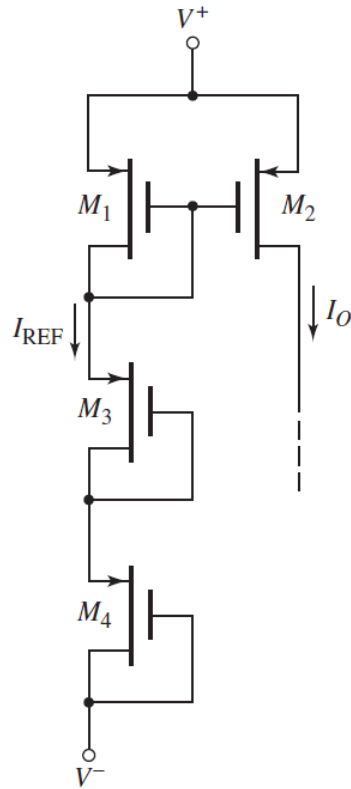


Figure 2: Problem 10.54

10.60 The transistors in the circuit shown in Figure P10.60 have parameters $V_{TN} = 0.4\text{V}$, $V_{TP} = -0.4\text{V}$, $k'_n = 100\mu\text{A}/\text{N}^2$, $k'_p = 60\mu\text{A}/\text{V}^2$, and $\lambda_n = \lambda_p = 0$. The transistor width-to-length ratios are $(W/L)_1 = e I_O/I_{\text{REF}}$, and $(W/L)_2 = 20$, $(W/L)_3 = 5$, and $(W/L)_4 = 10$. Determine $V_{DS2}(\text{sat})$. What are the values of V_{GS1} , V_{GS3} , and V_{SG4} ?

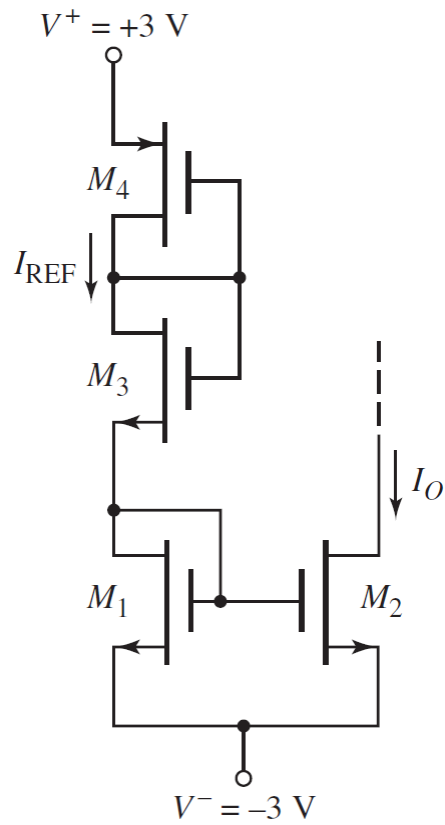


Figure 3: Problem 10.60

10.84 In the circuit in Figure P10.84, the active load circuit is replaced by Wilson current source. Assume that $\beta = 80$ for all transistors, and that $I_{\text{REF}} = 0.2\text{ mA}$. Determine the open-circuit small-signal voltage gain.

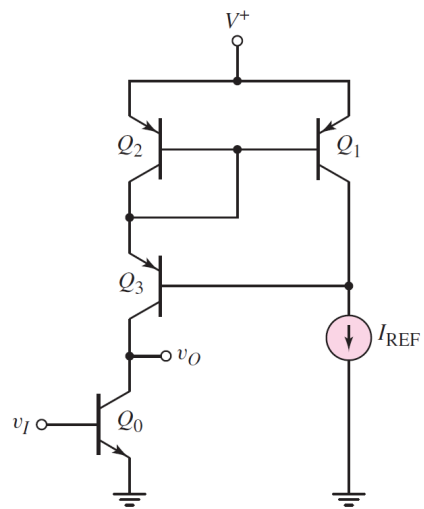


Figure 4: Problem 10.84