

# Microelectronics Circuit Analysis and Design

## Homework(8th)

Yuejin Xie U202210333

Oct 10th, 2023

- 5.24 (a) For the circuit in Figure P5.24, determine  $V_B$  and  $I_E$  such that  $V_B = V_C$ . Assume  $\beta = 90$ .  
 (b) What value of  $V_B$  results in  $V_{CE} = 2V$ ?

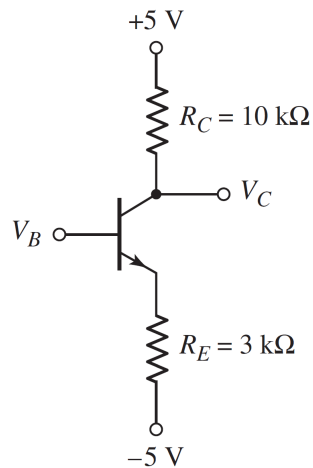


Figure 1: Problem 5.24

Solution:

- (a) Assume the BJT works in the forward-active region:

$$\begin{cases} I_C = \frac{5 - V_C}{R_C} \\ I_E = \frac{V_B - V_{BE(on)} - (-5)}{R_E} \\ I_E = \frac{1 + \beta}{\beta} I_C \\ V_B = V_C \end{cases} \Rightarrow \begin{cases} V_B = -2.14V \\ I_E = 0.72mA \end{cases}$$

(b) Obviously, the BJT work in the active region, so we have equation:

$$\begin{cases} V_C - V_B + V_{BE(on)} = V_{CE} \\ I_C = \frac{5 - V_C}{R_C} \\ I_E = \frac{V_B - V_{BE(on)} - (-5)}{R_E} \\ I_E = \frac{1 + \beta}{\beta} I_C \end{cases} \Rightarrow \begin{cases} V_B = -2.44\text{V} \\ I_E = 0.62\text{mA} \end{cases}$$

5.43 The common-emitter current gain of the transistor in Figure P5.43 is  $\beta = 80$ . Plot the voltage transfer characteristics over the range  $0 \leq V_I \leq 5\text{V}$ .

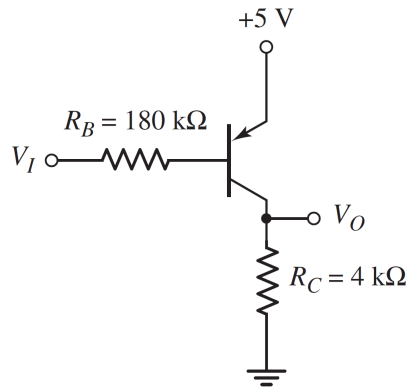


Figure 2: Problem 5.43

Solution:

It's a PNP BJT

case 1:  $V_I \in (4.3, 5)$ ,  $V_{EB} < 0.7\text{V}$ , the B-E junction isn't conducted,  $I_E = 0$ ,  $V_O = 0$

case 2: When BJT works in saturation region(at sat-point),  $V_{EC} = 0.2\text{V}$ ,  $V_O = 4.8\text{V}$ ,  $V_I = 5 - V_{EC(ON)} - \frac{V_O}{\beta R_C} R_B = 1.6\text{V}$ , so when  $V_I < 1.6\text{V}$ ,  $V_O = 4.8\text{V}$

case 3:  $V_I \in [1.6, 4.3]$ , the BJT works in the active region:

$$\frac{V_O}{R_C} = \beta \frac{5 - V_{BE(ON)} - V_I}{R_B} \Rightarrow V_O = -\frac{16}{9} V_I + \frac{344}{45}$$

5.70 For the circuit in Figure P5.70, let  $R_C = 2.2\text{k}\Omega$ ,  $R_E = 2\text{k}\Omega$ ,  $R_1 = 10\text{k}\Omega$ ,  $R_2 = 20\text{k}\Omega$ , and  $\beta = 60$ . (a) Find  $R_{TH}$  and  $V_{TH}$  for the base circuit. (b) Determine  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_E$ , and  $V_C$ .

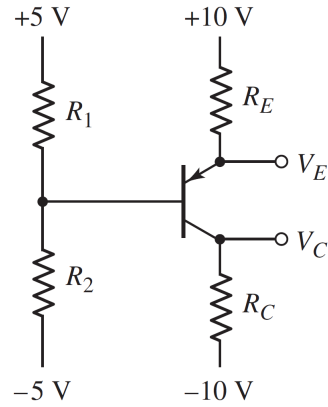


Figure 3: Problem 5.70

6.8 The parameters of each transistor in the circuits shown in Figure P6.8 are  $\beta = 130$ ,  $V_A = 80\text{V}$ , and  $I_{CQ} = 0.2\text{mA}$ . Determine the output resistance  $R_o$  for each circuit.

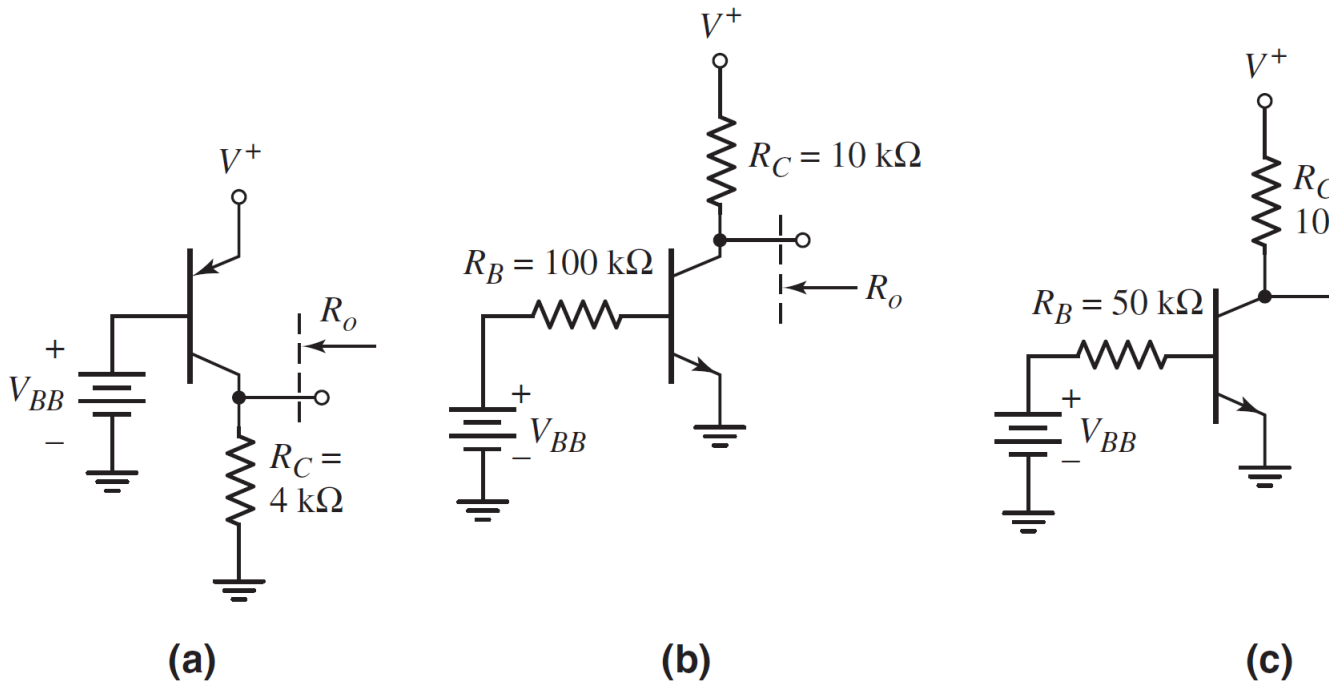


Figure 4: Problem 6.8

6.18 The signal source in Figure P6.18 is  $v_s = 5 \sin \omega t \text{ mV}$ . The transistor parameters are

$\beta = 120$  and  $V_A = \infty$ . (a) (i) Design the circuit such that  $I_{CQ} = 0.25\text{mA}$  and  $V_{CEQ} = 3\text{V}$ . (ii) Find the small-signal voltage gain  $A_v = v_o/v_s$ . (iii) Find  $v_o(t)$ . (b) Repeat part (a) for  $R_S = 0$ .

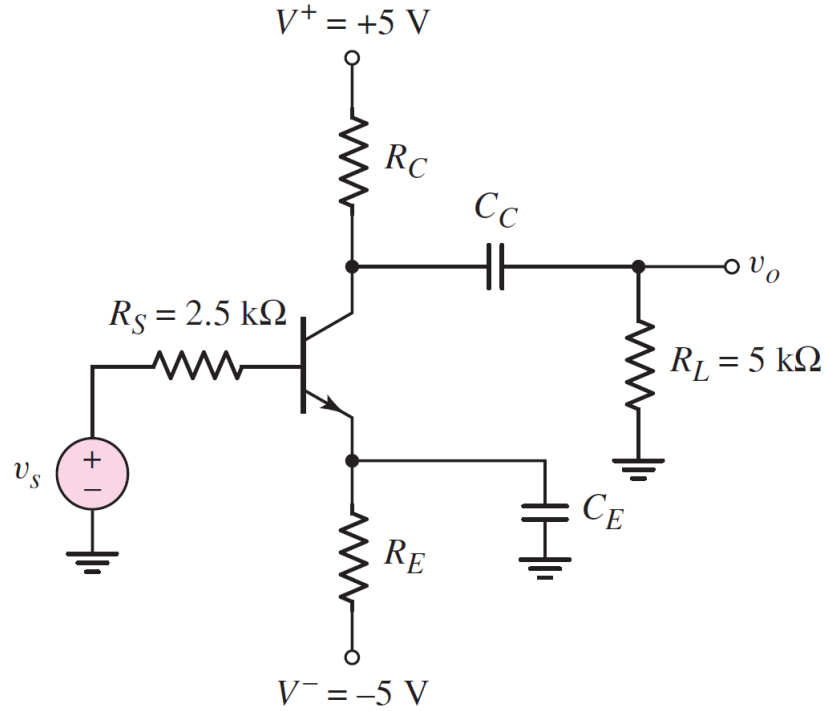


Figure 5: Problem 6.18

6.33 For the circuit in Figure P6.15, let  $\beta = 100$ ,  $V_A = \infty$ ,  $R_E = 12.9\text{k}\Omega$ , and  $R_C = 6\text{k}\Omega$ . Determine the maximum undistorted swing in the output voltage if the total instantaneous C–E voltage is to remain in the range  $1 \leq v_{CE} \leq 9\text{V}$  and if the total instantaneous collector current is to remain greater or equal to  $50\mu\text{A}$ .

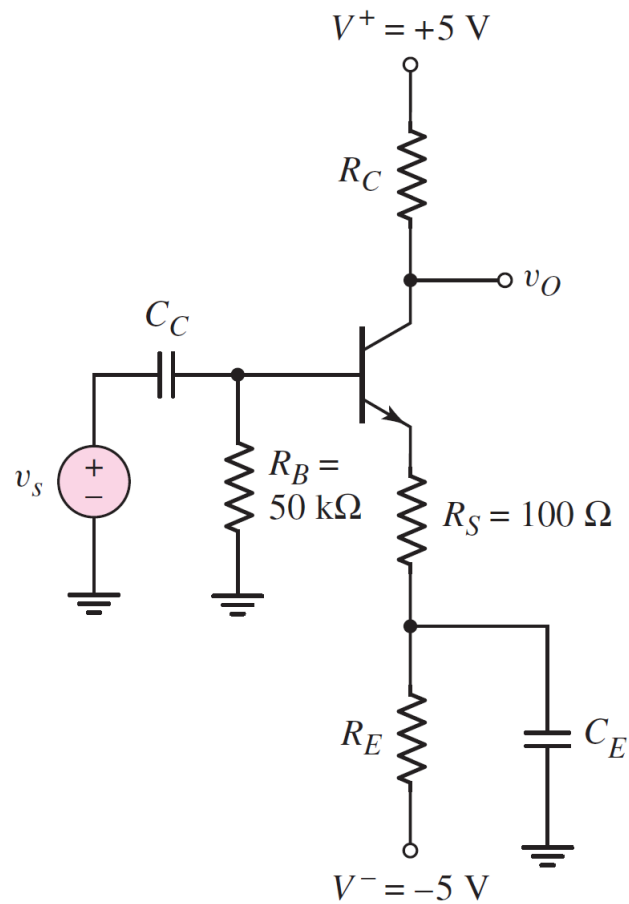


Figure 6: Problem 6.33

6.39 For the circuit in Figure P6.24, the transistor parameters are  $\beta = 100$  and  $V_A = \infty$ . (a) Determine the maximum undistorted swing in the output voltage if the total instantaneous E–C voltage is to remain in the range  $1 \leq v_{EC} \leq 9\text{ V}$ . (b) Using the results of part (a), determine the range of collector current.

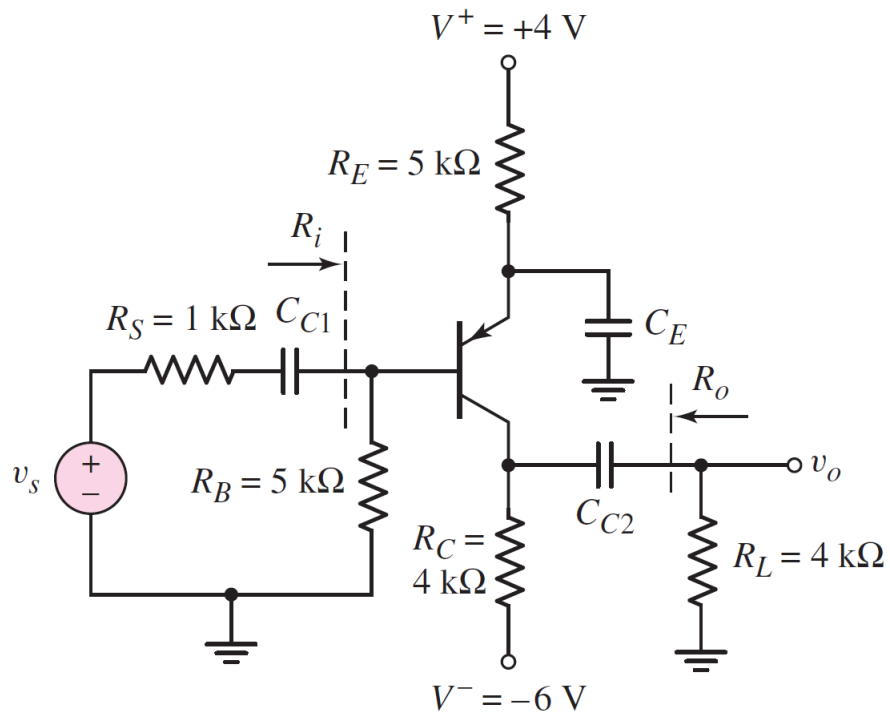


Figure 7: Problem 6.39

6.65 Consider the circuit shown in Figure P6.69. The transistor has parameters  $\beta = 60$  and  $V_A = \infty$ . (a) Determine the quiescent values of  $I_{CQ}$  and  $V_{CEQ}$ . (b) Determine the small-signal voltage gain  $A_v = v_o/v_s$ .

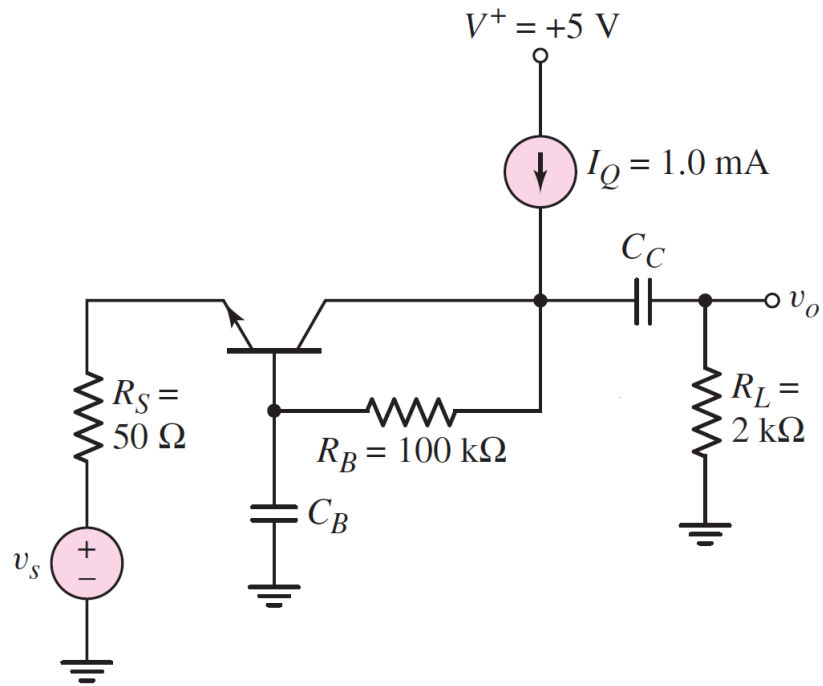


Figure 8: Problem 6.69