

Microelectronics Circuit Analysis and Design

Homework(2nd)

Yuejin Xie U202210333

Sept 5th, 2023

9.45 Consider the ideal noninverting op-amp circuit in Figure P9.45. (a) Derive the expression for v_O as a function of v_{I1} and v_{I2} . (b) Find v_O for $v_{I1} = 0.2V$ and $v_{I2} = 0.3V$. (c) Find v_O for $v_{I1} = +0.25V$ and $v_{I2} = -0.40V$.

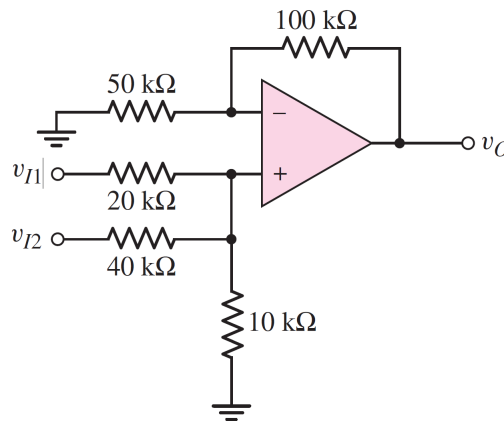


Figure 1: Problem 9.45

Solution:

(a) Because of "virtual short", "virtual open", we have equations as follow:

$$\begin{cases} \frac{v_{I1} - v_+}{20k\Omega} + \frac{v_{I2} - v_+}{40k\Omega} = \frac{v_+ - 0}{10k\Omega} \\ v_+ = v_- \\ \frac{0 - v_-}{50k\Omega} = \frac{v_- - v_O}{100k\Omega} \end{cases} \Rightarrow v_O = \frac{6v_{I1} + 3v_{I2}}{7} \quad (1)$$

(b) substitute $v_{I1} = 0.2V$ and $v_{I2} = 0.3V$ into the (1) $\Rightarrow v_O = 0.3V$

(c) substitute $v_{I1} = +0.25V$ and $v_{I2} = -0.40V$ into the (1) $\Rightarrow v_O = 42.86mV$

9.75 The circuit in Figure P9.75 is a first-order low-pass active filter. (a) Show that the voltage transfer function is given by

$$A_v = -\frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2}$$

(b) What is the voltage gain at dc ($\omega = 0$)? (c) At what frequency is the magnitude of the voltage gain a factor of $\sqrt{2}$ less than the dc value? (This is the -3 dB frequency.)

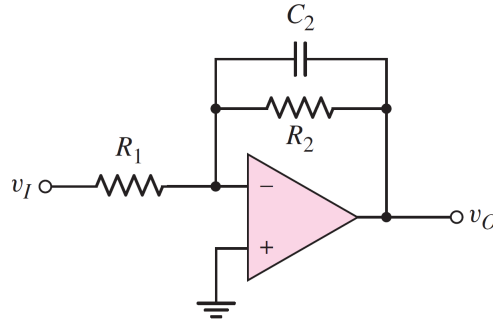


Figure 2: Problem 9.75

Solution:

(a) Because of "virtual short", "virtual open", we have equations as follow:

$$\begin{cases} \frac{v_I - v_-}{R_1} = \frac{v_- - v_O}{R_2} + \frac{v_- - v_O}{j\omega C_2} \\ v_+ = v_- = 0 \end{cases} \Rightarrow A_v = \frac{v_I}{v_O} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega R_2 C_2}$$

(b) when $\omega = 0$, $A_v(DC) = -\frac{R_2}{R_1}$

(c) $|A_v| = \frac{A_v(DC)}{\sqrt{2}} \Rightarrow \omega = \frac{1}{R_2 C_2} \Rightarrow f = \frac{1}{2\pi R_2 C_2}$