

Microelectronics Circuit Analysis and Design

Homework(14th)

Yuejin Xie U202210333

Nov 12nd, 2023

Analysis circuit, determine the voltage gain:

1.

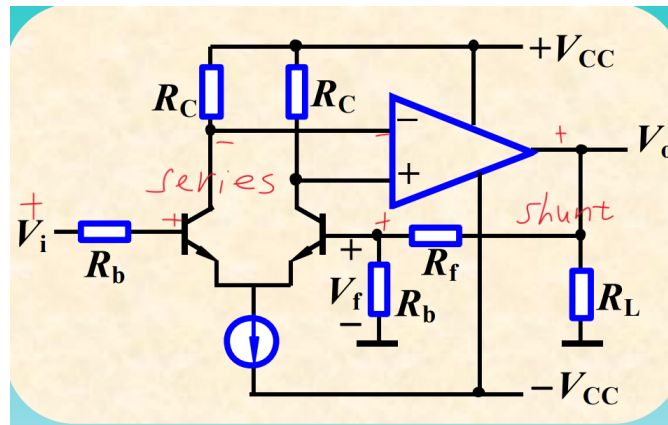


Figure 1: Problem 1

Solution:

It's a Series-Shunt-Negative Feedback Circuit. The voltage gain is as follow:

$$A_{vf} = \frac{V_o}{V_i} = \frac{V_o}{V_f} = \frac{V_o}{\frac{R_b}{R_f + R_b} V_o} = 1 + \frac{R_f}{R_b}$$

2.

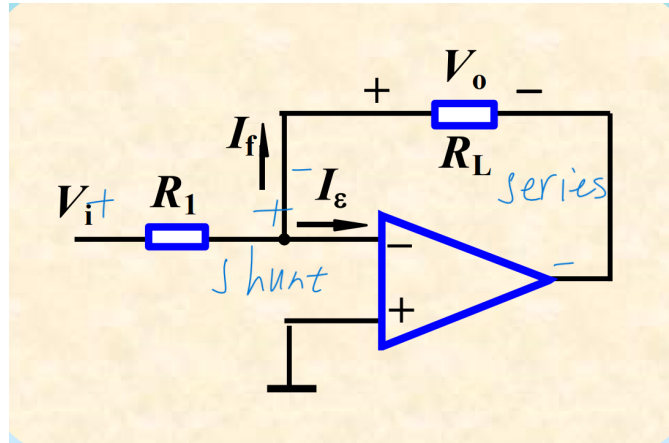


Figure 2: Problem 2

Solution:

It's a Shunt-Shunt-Negative Feedback Circuit. The gain is as follow:

$$A_{rf} = \frac{V_o}{I_i} = \frac{V_o}{I_f} = R_L \Rightarrow A_{vs} = \frac{V_o}{V_i} = \frac{V_o}{I_i R_1} = \frac{R_L}{R_1}$$

3.

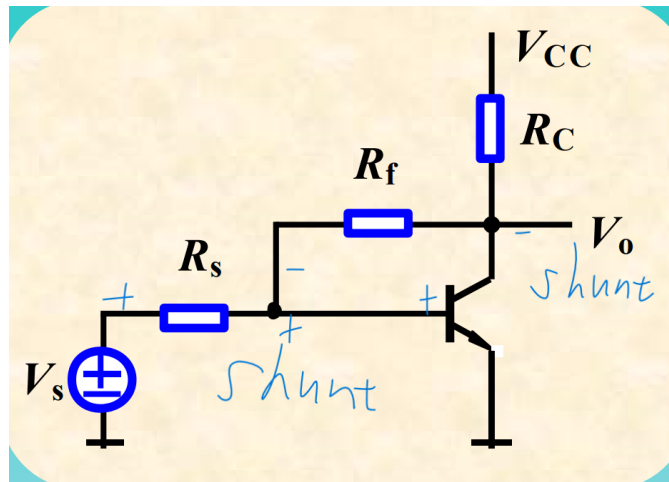


Figure 3: Problem 3

Solution:

It's a Shunt-Shunt-Negative Feedback Circuit. The gain is as follow:

$$A_{rf} = \frac{V_o}{I_i} = \frac{V_o}{I_f} = -R_f \Rightarrow A_{vs} = \frac{V_o}{V_i} = \frac{V_o}{I_i R_s} = -\frac{R_f}{R_s}$$

4.

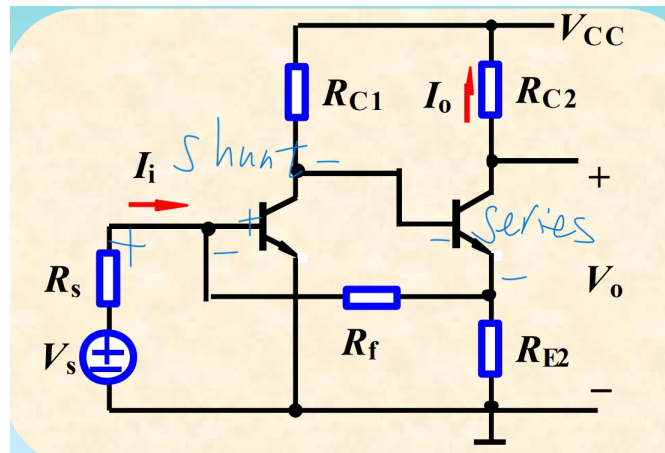


Figure 4: Problem 4

Solution:

It's a Shunt-Series-Negative Feedback Circuit. The gain is as follow:

$$A_{if} = \frac{I_o}{I_i} = \frac{I_o}{\frac{R_{E2}}{R_{E2} + R_f} I_o} = 1 + \frac{R_f}{R_{E2}} \Rightarrow A_{vs} = \frac{V_o}{V_i} = \frac{I_o R_{C2}}{I_i R_s} = \frac{R_{C2}}{R_s} \left(1 + \frac{R_f}{R_{E2}} \right)$$

5. Design feedback network determine its parameter, and connect it with basic amp. Assume that closed-loop is

$$A_{vf} = \frac{V_o}{V_i} = -47$$

