

# Microelectronics Circuit Analysis and Design

## Homework(4th)

Yuejin Xie U202210333

Sept 15th, 2023

2.14 The circuit in Figure P2.14 is a complementary output rectifier. If  $v_s = 26 \sin[2\pi(60)t]\text{V}$ , sketch the output waveforms  $v_o^+$  and  $v_o^-$  versus time, assuming  $V_\gamma = 0.6\text{V}$  for each diode.

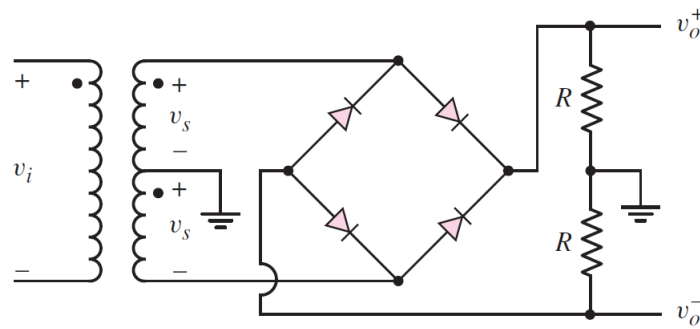


Figure 1: Problem 2.14


Solution:

The four diodes from left to right and top to bottom are numbered A, B, C, and D respectively.

When  $0 < t \leq \frac{T}{2}$ , A, C are conducted and B, D aren't, so at this moment,  $v_o^+ = v_s - V_\gamma$ ,  $v_o^- = -v_s + V_\gamma$  (conducted, if aren't conducted  $v_o^+ = v_o^- = 0$ )

When  $\frac{T}{2} < t < T$ , B, D are conducted and A, C aren't, so at this moment, the answer is the same as  $0 < t \leq \frac{T}{2}$

We provide results using Multisim:

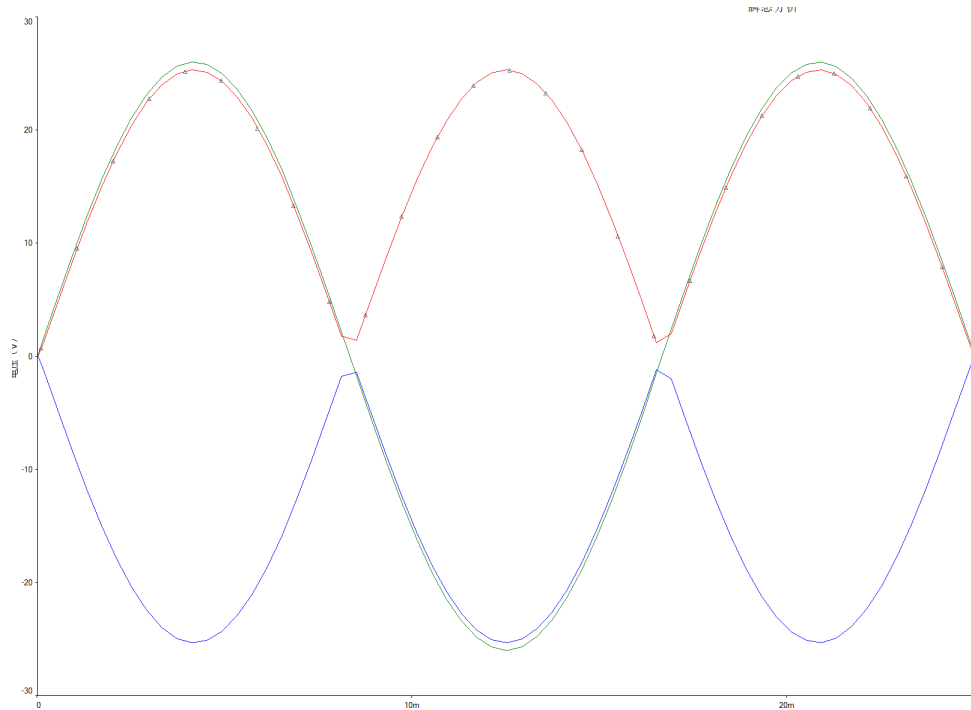

2.45 In the circuit in Figure P2.45 the diodes have the same piecewise linear parameters as described in Problem 2.44 ( $V_\gamma = 0.6\text{V}$  and  $r_f = 0$ ). Calculate the output voltage  $V_O$  and the currents  $I_{D1}$ ,  $I_{D2}$ , and  $I$  for the following input conditions: (a)  $V_1 = V_2 = 10\text{V}$ ; (b)  $V_1 = 10\text{V}$ ,  $V_2 = 0$ ; (c)  $V_1 = 10\text{V}$ ,  $V_2 = 5\text{V}$ ; and (d)  $V_1 = V_2 = 0$ .

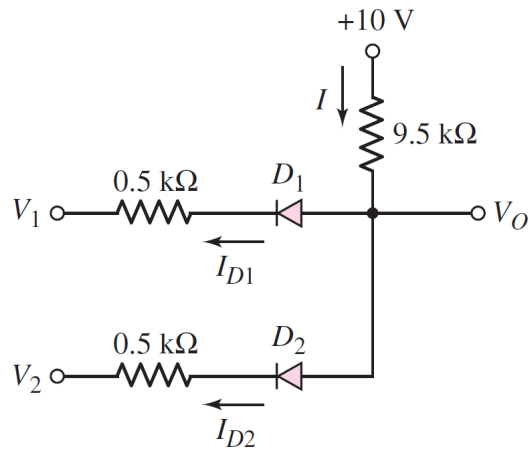


Figure 2: Problem 2.45

Solution:

(a) Owing to  $V_s = V_1 = V_2 = 10V$ ,  $D_1$  and  $D_2$  can't be conducted, so  $V_O = V_s = 10V$ ,  $I = I_{D1} = I_{D2} = 0$ ,

(b) In this case,  $D_2$  is conducted but  $D_1$  not, so  $I_{D1} = 0$ ,  $I_{D2} = I = \frac{V_s - V_\gamma}{R_1 + R_2} = 0.94mA$ .  
 $V_O = V_s - IR_1 = 1.07V$

(c) In this case,  $D_2$  is conducted but  $D_1$  not, so  $I_{D1} = 0$ ,  $I_{D2} = I = \frac{V_s - V_\gamma}{R_1 + R_2} = 0.44mA$ .  
 $V_O = V_s - IR_1 = 5.82V$

(d) In this case, both  $D_1$  and  $D_2$  are conducted, we have equation:

$$\begin{cases} I = \frac{V_s - V_O}{R_1} \\ I = I_{D1} + I_{D2} \\ I_{D1} = I_{D2} = \frac{V_O - V_\gamma}{R_1} \end{cases} \Rightarrow \begin{cases} I = 0.964mA \\ V_O = 0.842V \\ I_{D1} = I_{D2} = 0.482mA \end{cases}$$

2.58 (a) Each diode in the circuit in Figure P2.58 has piecewise linear parameters of  $V_\gamma = 0$  and  $r_f = 0$ . Plot  $v_O$  versus  $v_I$  for  $0 \leq v_I \leq 30V$ . Indicate the breakpoints and give the state of each diode in the various regions of the plot. (b) Compare the results of part (a) with a computer simulation analysis.

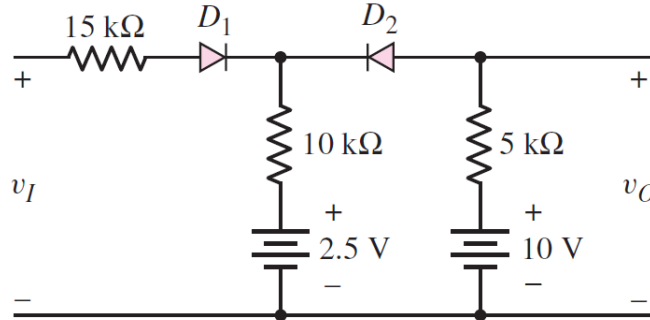


Figure 3: Problem 2.58

Solution:

(a) When  $0 < V_I < 2.5V$ ,  $D_1$  and  $D_2$  aren't conducted, so  $V_O = 10V$

When  $2.5V \leq V_I < 21.25V$ ,  $D_1$  is conducted but  $D_2$  not, so  $V_O = 10V$

When  $21.25V \leq V_I < 30V$ ,  $D_1$  and  $D_2$  are conducted, we have equation:

$$\frac{V_I - V_O}{15k\Omega} = \frac{V_O - 2.5}{10k\Omega} + \frac{V_O - 10}{5k\Omega}$$

$$\Rightarrow V_O = \frac{2}{11}V_I + \frac{135}{22}$$

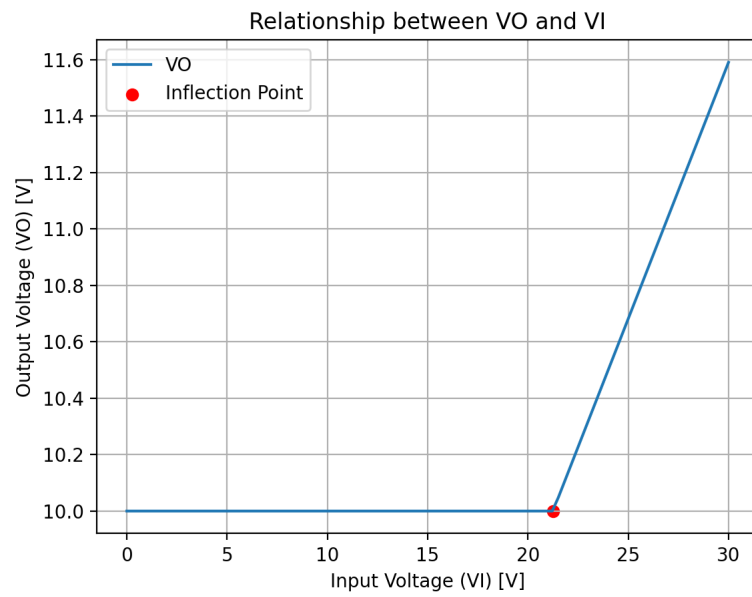


Figure 4:  $v_O$  versus  $v_I$  for  $0 \leq v_I \leq 30V$

(b)

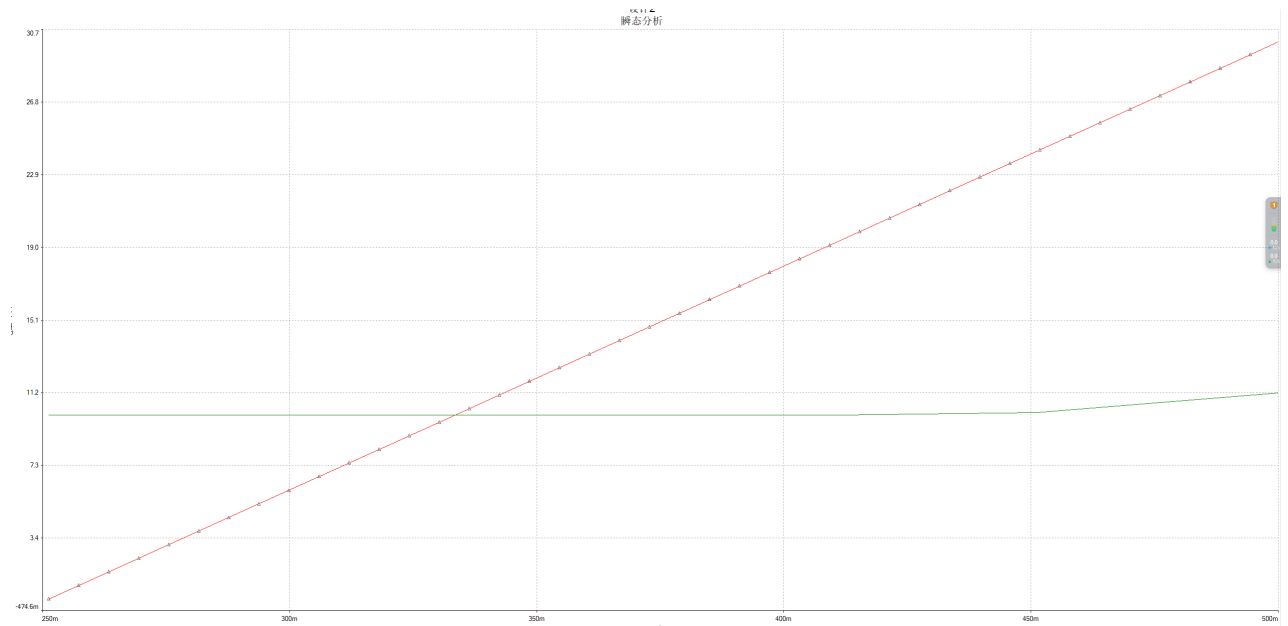


Figure 5: Multisim AAAnalysis