

Microelectronics Circuit Analysis and Design

Homework(6th)

Yuejin Xie U202210333

Sept 27th, 2023

4.15 For the NMOS common-source amplifier in Figure P4.15, the transistor parameters are: $V_{TN} = 0.8\text{V}$, $K_n = 1\text{mA/V}^2$, and $\lambda = 0$. The circuit parameters are $V_{DD} = 5\text{V}$, $R_S = 1\text{k}\Omega$, $R_D = 4\text{k}\Omega$, $R_1 = 225\text{k}\Omega$, and $R_2 = 175\text{k}\Omega$. (a) Calculate the quiescent values I_{DQ} and V_{DSQ} . (b) Determine the small-signal voltage gain for $R_L = \infty$. (c) Determine the value of R_L that will reduce the small-signal voltage gain to 75 percent of the value found in part (b).

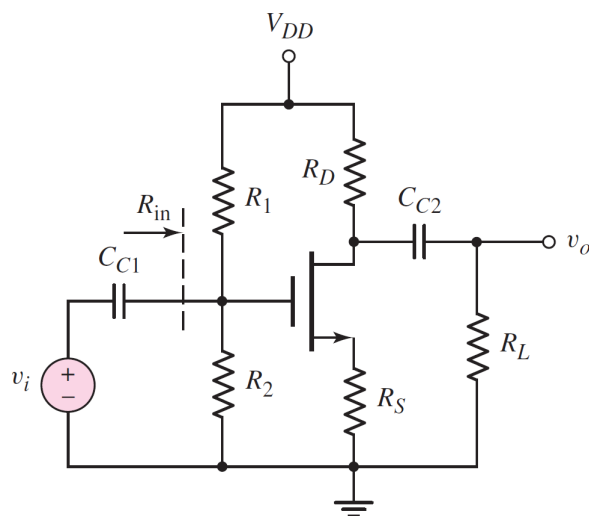


Figure 1: Problem 4.15/4.17

Solution:

$$(a) V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{35}{16} \text{V}, \text{ assume that the transistor work in the saturation region:}$$

$$V_S = I_D R_S, I_D = K_n (V_G - V_S - V_{TN})^2 \Rightarrow I_D = 0.61\text{mA or } 3.17\text{mA (Ignore)}$$

$$\therefore V_{GS} = V_G - V_S = 1.58V, V_{DSQ} = V_{DD} - I_D R_D = 1.96V > V_{GS} - V_{TN}$$

(b) $R_L = \infty \Leftrightarrow$ Circuit is open, so the equivalent circuit is as follow:

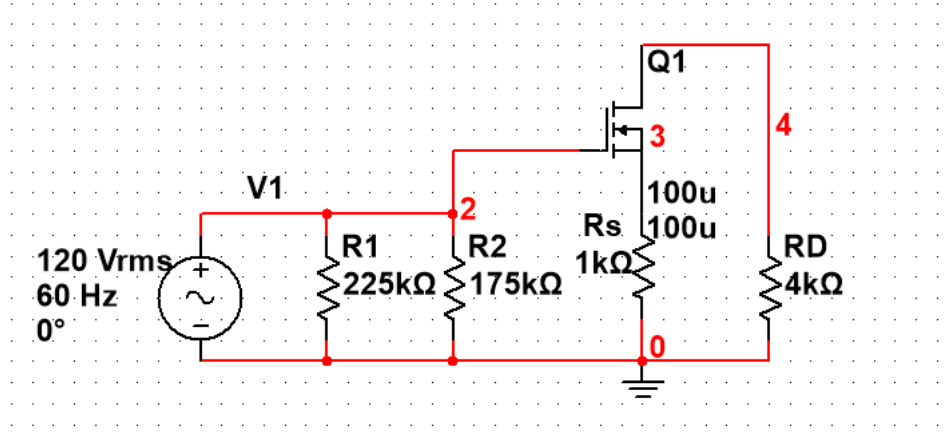


Figure 2: Problem 4.15

$$g_m = 2K_n(V_{GSQ} - V_{TN}) = 1.56\text{mS}, i_d = g_m v_{gs}, v_o = -i_d R_D, A_v = \frac{v_o}{v_{gs}} = -2.44$$

$$(c) A'_v = 0.75 A_v = \frac{-i_d (R_L || R_D)}{v_{gs}} \Rightarrow R_L = 12\text{k}\Omega$$

4.17 Repeat Problem 4.15 if the source resistor is bypassed by a source capacitor C_S .

(a) The answer is the same as 4.15(a), because in the case of DC, the source capacitor is open, answer doesn't change.

$$I_D = 0.61\text{mA}, V_{DSQ} = 1.96\text{V}$$

(b)(c) In this case, the R_S is shorted, but i_d doesn't change, so the answer is the same as 4.15(b)(c)

$$\therefore (b) A_v = -2.44 \quad (c) R_L = 12\text{k}\Omega$$

D4.26 Design the common-source circuit in Figure P4.26 using an n-channel MOSFET with $\lambda = 0$. The quiescent values are to be $I_{DQ} = 6\text{mA}$, $V_{GSQ} = 2.8\text{V}$, and $V_{DSQ} = 10\text{V}$. The transconductance is $g_m = 2.2\text{mA/V}$. Let $R_L = 1\text{k}\Omega$, $A_v = -1$, and $R_{in} = 100\text{k}\Omega$. Find R_1, R_2, R_S, R_D, K_n , and V_{TN} .

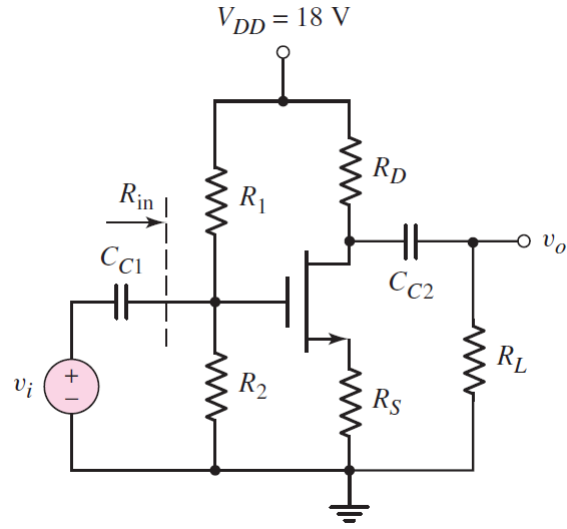


Figure 3: Problem 4.26

Solution:

Obviously, the transistor is work in the saturation region, we have equation:

$$\left\{ \begin{array}{l} I_{DQ} = K_n (V_{GSQ} - V_{TN})^2 \\ V_{DSQ} = V_{DD} - I_D R_D \\ V_G = \frac{R_2}{R_1 + R_2} V_{DD} \\ V_S = I_D R_S \\ g_m = 2K_n (V_{GSQ} - V_{TN}) \\ R_{in} = \frac{R_1 R_2}{R_1 + R_2} \\ A_v = \frac{-g_m v_{gs} (R_D || R_L)}{v_{gs}} \end{array} \right. \Rightarrow \left\{ \begin{array}{l} R_1 = \\ R_2 = \\ R_S = \\ R_D = \\ K_n = \\ V_{TN} = \end{array} \right.$$