

Microelectronics Circuit Analysis and Design

Homework(5th)

Yuejin Xie U202210333

Sept 21st, 2023

3.27 The transistor in the circuit in Figure P3.27 has parameters $V_{TN} = 0.8\text{V}$ and $K_n = 0.25\text{ mA/V}^2$. Sketch the load line and plot the Q -point for (a) $V_{DD} = 4\text{V}$, $R_D = 1\text{k}\Omega$ and (b) $V_{DD} = 5\text{V}$, $R_D = 3\text{k}\Omega$. What is the operating bias region for each condition?

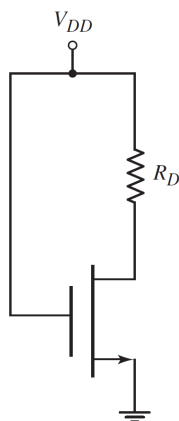


Figure 1: Problem 3.27

Solution:

(a) Assume the transistor works in the saturation region:

$$V_{GS} = V_{DD} = 4\text{V} \Rightarrow i_d = K_n(V_{GS} - V_{TN})^2 = 2.56\text{mA}.$$

$\therefore V_{DS} = V_{DD} - i_d R_D = 1.44\text{V} < V_{GS} - V_{TN} \Rightarrow$ the transistor works in the nonsaturation region

$$\therefore \begin{cases} i_d = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2] \\ V_{DS} = V_{DD} - i_d R_D \end{cases} \Rightarrow \begin{cases} i_d = 2.12\text{mA} \\ V_{DS} = 1.88\text{V} \end{cases}$$

(b) Assume the transistor works in the saturation region:

$$V_{GS} = V_{DD} = 4V \Rightarrow i_d = K_n(V_{GS} - V_{TN})^2 = 4.41\text{mA}.$$

$\therefore V_{DS} = V_{DD} - i_d R_D = -8.23\text{V} < V_{GS} - V_{TN} \Rightarrow$ the transistor works in the nonsaturation region:

$$\therefore \begin{cases} i_d = K_n [2(V_{GS} - V_{TN})V_{DS} - V_{DS}^2] \\ V_{DS} = V_{DD} - i_d R_D \end{cases} \Rightarrow \therefore \begin{cases} i_d = 1.42\text{mA} \\ V_{DS} = 0.741\text{V} \end{cases}$$

3.35 For the transistor in the circuit in Figure P3.35, the parameters are $V_{TN} = 0.4\text{ V}$, $k'_n = 120\mu\text{A/V}^2$, and $W/L = 25$. Determine V_{GS} , I_D , and V_{DS} . Sketch the load line and plot the Q-point.

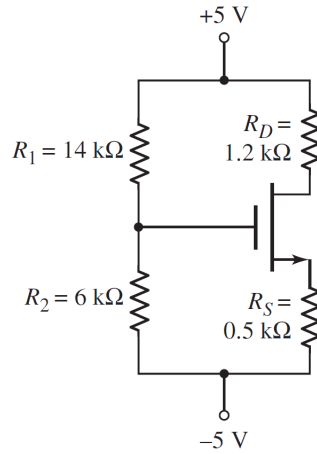


Figure 2: Problem 3.35

Solution:

$$\text{Actually, } K_n = \frac{k'_n}{2} \cdot \frac{W}{L} = 1.5\text{mA/V}^2$$

Assume the transistor works in the saturation region:

$$V_G = \frac{R_2}{R_1 + R_2}(V_{DD} - V_{SS}) + V_{SS} = -2\text{V}, V_S = I_D R_S + V_{SS} = (0.5I_D - 5)\text{V}$$

$$\therefore I_D = K_n(V_G - V_S - V_{TN})^2 \Rightarrow I_D = 2.58\text{mA} \text{ or } 10.49\text{mA (Ignore)}$$

$$\therefore V_{GS} = V_G - V_S = 1.71\text{V}, V_{DS} = V_{DD} - I_D R_D - V_S = 5.61\text{V}.$$